
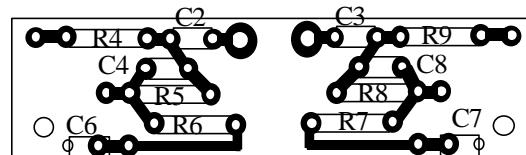



INPUT BOARD

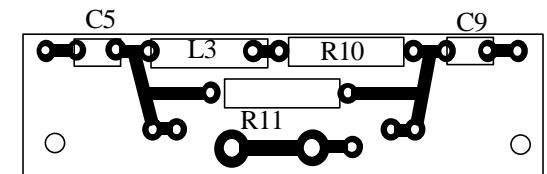


FIRST STAGE INPUT




FIRST STAGE OUTPUT

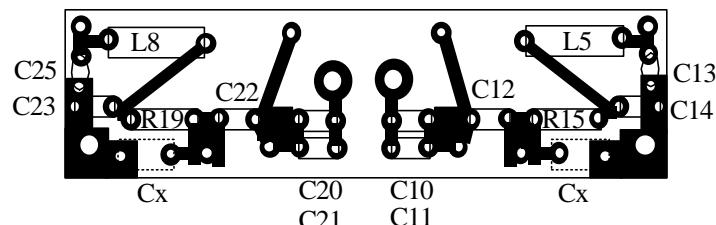


SECOND STAGE INPUT

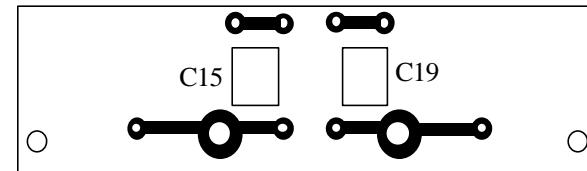

SECOND STAGE OUTPUT

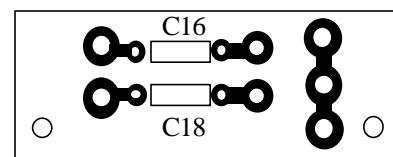

COAX OUTPUT

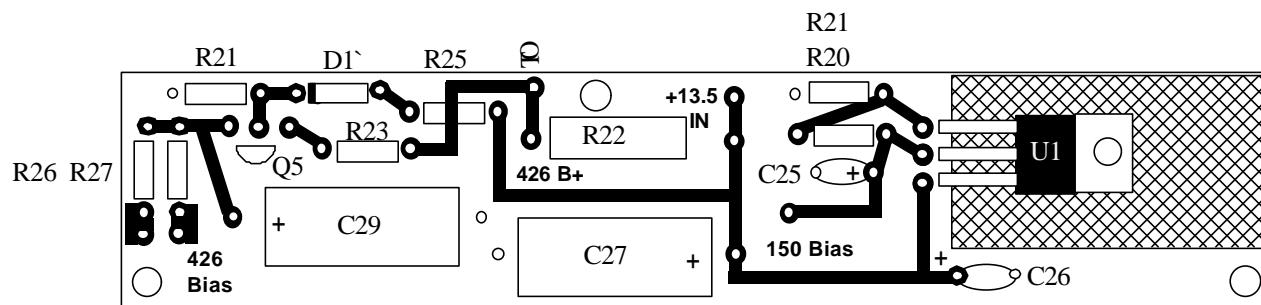

REGULATOR

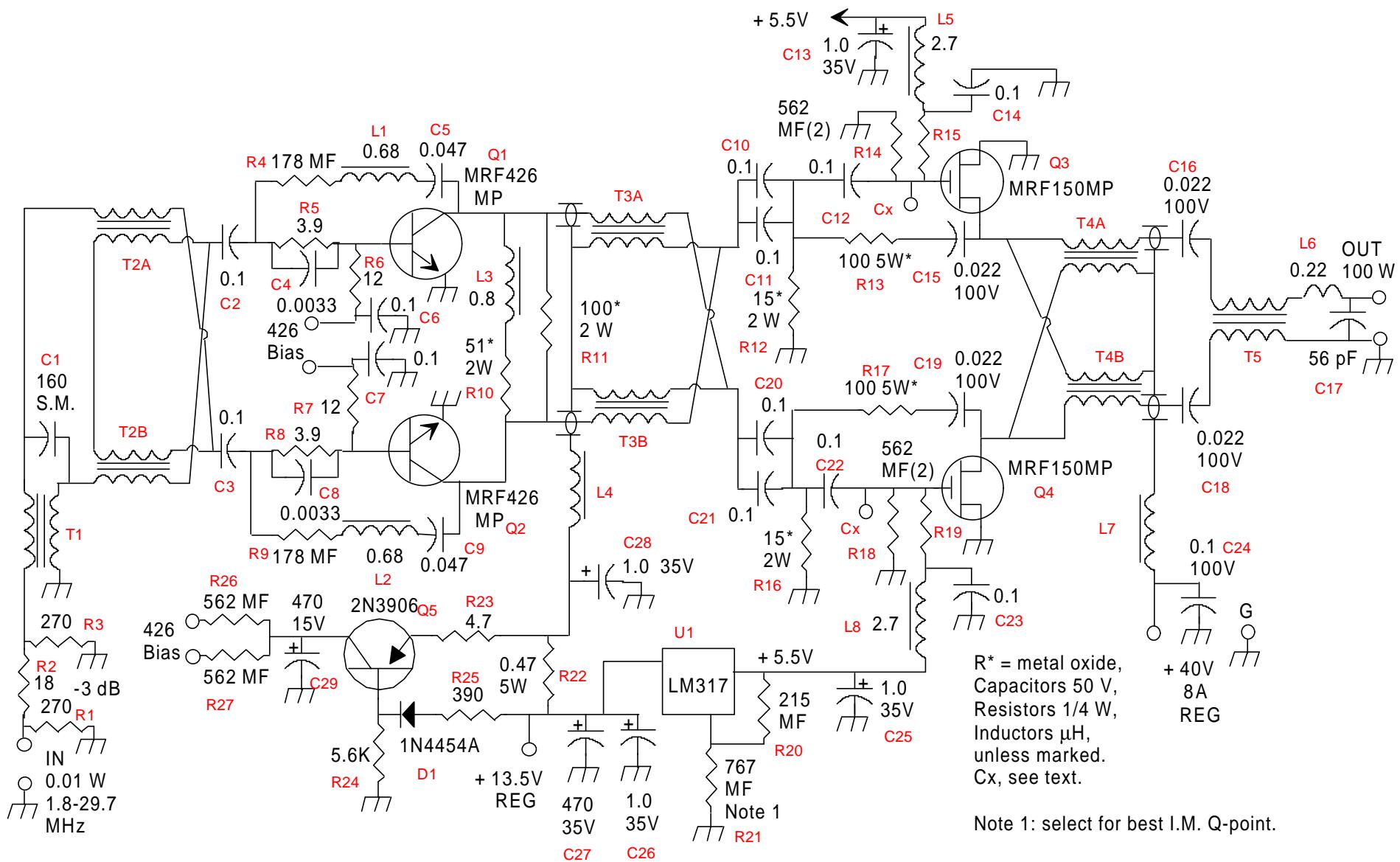


Figure 5. Schematic diagram of two-stage 100 watt amplifier.