

# Hybrid HF Transmitter

**This single-band design mixes solid state circuitry with vacuum tube final amplifiers.**

## Yosef Pinhasi, 4Z1VC

The single sideband (SSB) transmitter shown on the left side of Figure 1 is a hybrid of solid state devices and two vacuum tubes in the RF power stage, designed to operate upper SSB phone in the 20 meter band. You can easily modify it to work in another band and to add lower SSB. I kept the design simple and compact by using integrated devices and direct coupling. Each printed circuit board has its own power supply and voltage regulation circuitry. For electromagnetic compatibility, I separated the RF power stages from the VFO and receiving sections (the cabinet on the right side of Figure 1).

Figure 2 shows a block diagram of the entire transceiver incorporating the transmitter described here, and identifies signal connections A – D, which are referenced in the schematics. The receiver (not described in detail) is a single conversion superheterodyne design based on the SA605 mixer. This article focuses on the transmitter section. The transmitter consists of the Motorola MC1496 balanced modulator, which generates a double sideband signal at the 455 kHz IF, a band-pass SSB filter, upconversion SA602 balanced mixer, pre-driver transistors, 12BY7A driver pentode, and 6146B power beam tetrode final, producing 25 to 30 W PEP. The transmitter and receiver share a DDS VFO. *You should be very careful and take all necessary precautions due to the dangerous high voltages involved.*

### Balanced Modulator

The modulator schematic diagram (Figure 3) uses a Motorola MC1496 balanced modulator IC.<sup>1</sup> A photo of the modulator board and additional relevant photos can be found on the *QST* in Depth web page.<sup>2</sup>



**Figure 1** — Hybrid transmitter (left) and VFO/receiver (right). The transmitter knobs upper row (left to right) are Band Selector (optional), and Microphone Level; knobs lower row (left to right) are Load Capacitor, Plate Capacitor, Metering Selector (optional); switches (left to right) are Tone, 12 V, TR, 500 V, 250 V, Power off/on; input jacks are Auxiliary (left), and Microphone (right).


Audio signals from microphone, external auxiliary line or internal tone generator are combined in operational amplifier U103. The MICROPHONE signal feeds Q105, enabling use of a standard 600  $\Omega$  dynamic or an electrostatic microphone. The gain of the microphone pre-amplifier can be adjusted by R114, which sets the modulation level. Phase-shift oscillator Q106 generates a tone of approximately 1 kHz. This TONE oscillator can be switched ON (S101) for transmitter testing and tuning. Trimmer R133 sets the tone modulation level. An AUXILIARY input allows signals from an external audio device, such as a computer line-out. The impedance is 47 k $\Omega$ , similar to that of standard audio inputs. The voltage gain of U103 is four, producing 500 mV peak to the signal input of balanced modulator U102.

Modulator U102 generates a DSB suppressed-carrier signal centered on 452 kHz (3 kHz below the mid frequency of the SSB filter). Since this is the lower edge of

the piezoelectric ceramic band-pass filter Y102 (mounted on a small PC board on the modulator board), the lower sideband is removed, resulting in the upper sideband at A.

BFXO Q101 produces the 452 kHz sub-carrier. I used a common 455 kHz ceramic resonator and warped its frequency with capacitor pair C101 and C102. Find the appropriate value of C102 that lets C101 adjust the oscillation frequency to 452 kHz. Two stage amplifier Q102 and Q103 buffers the BFXO output and delivers a 100 mV peak 452 kHz IF sine wave to the balanced modulator. The BFXO buffer and balanced modulator U102 are switched on only during transmission when 12 V dc from the power amplifier TR circuitry appears at point C, the base of Q104. This mutes the RF signals during reception. Adjust trimmer R128 for best carrier null at the output. The peak voltage of the SSB signal at the filter output A is 500 mV.

<sup>1</sup>Notes appear on page 39.

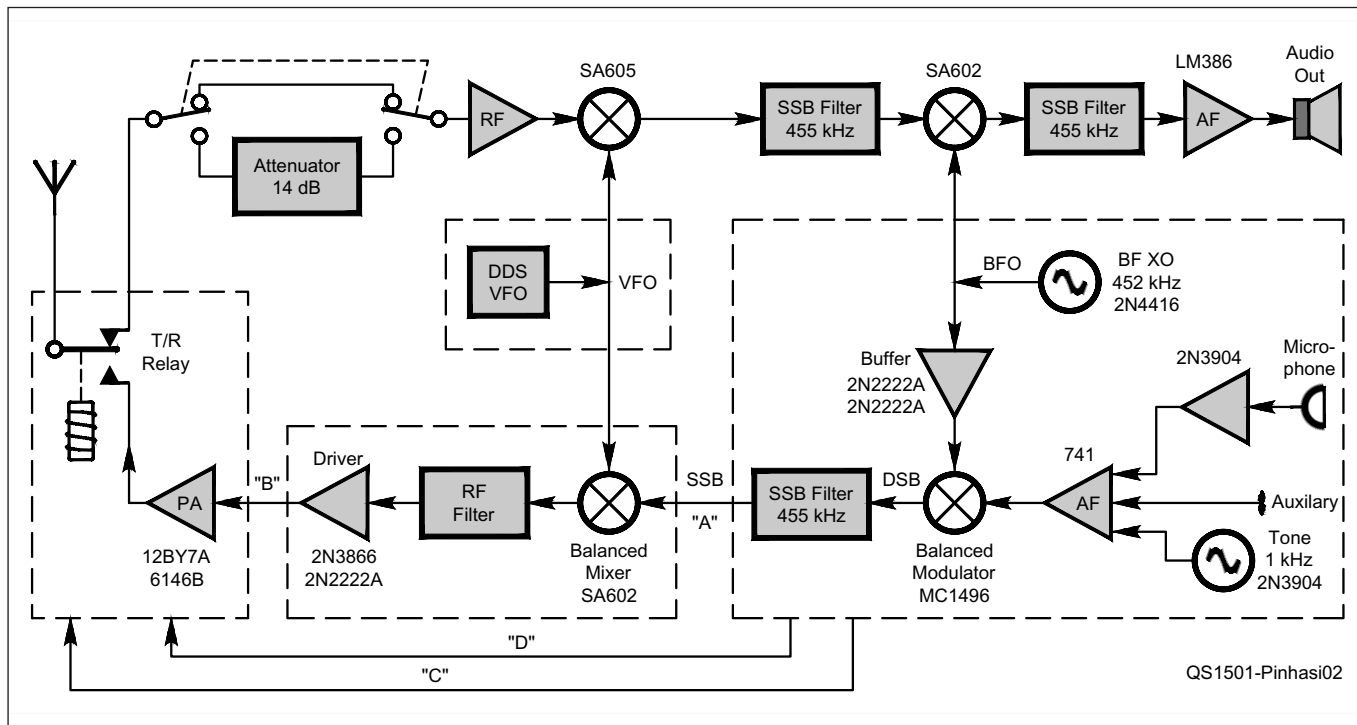

**Figure 2** — Block diagram of the transceiver showing circuit block connections. The transmitter includes (lower right to left) the audio section; the BFO, buffer amps, and balanced modulator; SSB filter; DDS VFO, balanced mixer with RF filter and driver; and the tube RF power amplifier with TR switch.

### Upconversion Mixer

U202 (Figure 4) supplies 6 V to the upconversion double-balanced mixer U201.<sup>3</sup> The SSB, suppressed-carrier signal A from Y102 feeds Pin 1 of U201 via C202 and R202. U201 has an internal local oscillator, but my attempts to build a VFO around it led to frequency instabilities and drift.<sup>4</sup> Instead, I used the DDS-2 kit from D. C. Pongrance, N3ZI, as the transceiver VFO.<sup>5</sup> After amplification, it produces a 1 V P-P pure sine wave at the difference between the radio frequency and the 452 kHz intermediate frequency. The DDS signal feeds Pin 6 of the upconversion mixer U201 via C201 and R201. Adjust trimmer R204 for best carrier null at output B. The band-pass network following the mixer output is centered at 14.128 MHz.

### Power Amplifier

The RF power amplifier stage shown in Figure 5 is based on pentode driver V301 followed by beam power tetrode V302. Here, the plate voltage is set to 250 V and the screen voltage is regulated to 150 V by 5 W Zener diode D306, resulting in a total cathode current of about 30 mA.

The 30–40 V peak RF signal from driver

V301 feeds the grid of V302 through a parallel resonant network tuned to the center of the band. The high Q of the circuit helps remove the image products from the upconversion mixer, and suppresses parasitic oscillations that may result from instabilities. Neutralization was not necessary in this design. The resonant frequency of the parallel LC circuit (C310 and L303) is set to the center of the 20 meter amateur band. Set the GRID trimmer capacitor C310 for maximum amplitude of the driving signal when the V302 is installed, but the transmit switch is OFF.

V302 operates as a class AB<sub>1</sub> linear power amplifier. The dc plate voltage can be set either to 250 V for low level 2–5 W output or to 500 V for 30 W PEP. The screen voltage is 200 V regulated by 5 W Zener diode D307. The grid bias is fixed to –48 V, resulting in about 20–30 mA cathode quiescent current. The output Pi network converts the 50 Ω load to the impedance required by V302. For the 20 meter band, tank inductor L305 is seven turns of #16 AWG enameled wire on a 3.6 cm diameter plastic cylinder. It can be seen up against the front panel in Figure 6. High voltage is supplied to the anode of V302 through RF choke L302, which must handle at least

250 mA. The parasitic suppressor L306 is wound on 1 W resistor R307.

V302 cathode current is measured by a 1 mA dc milliammeter connected in parallel with R309 cathode resistor via R310, producing a maximum scale reading of 200 mA.

I placed my transmitter chassis in a ventilated cabinet made of a transparent thermoplastic. [You may wish to use a ventilated metal enclosure to minimize RF leakage and to reduce exposure to RF. — Ed.]

### TR Relay

Transmit/receive relay K301 is controlled by voltage signal D from the modulator board (the upper board seen in Figure 6). During transmission, signal D from Q104 to opto-coupler Q301 activates relay K301, connecting the antenna to the output of the power amplifier and shorting the receiver connection to ground. Opto-coupler Q302 drives an open collector transistor Q303 to produce a TR indicator for the receiver (or for an external high power linear amplifier). The TR circuit is mounted on the mixer PC board (lower board seen in Figure 6) and uses the same 12 V regulator U203.


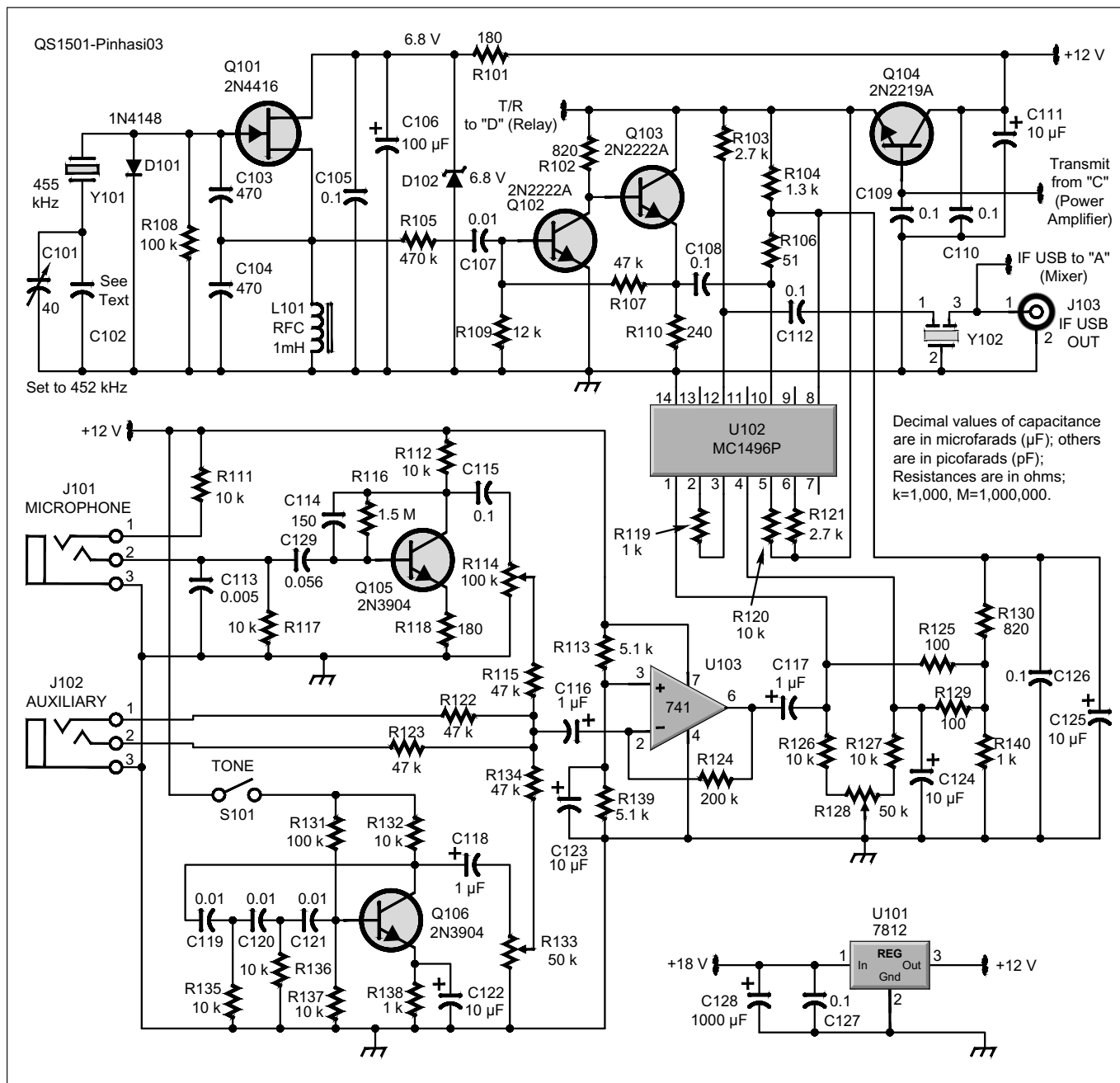


Figure 3 — Audio input, beat frequency oscillator, balanced modulator, and SSB filter schematic.

C101 — 40 pF variable capacitor  
 C102 — (see the "Balanced Modulator" section of the text)  
 C103, C104 — 470 pF capacitor  
 C105, C108 — C110, C112, C115, C126, C127 — 0.1 μF capacitor  
 C106 — 100 μF capacitor  
 C107, C113, C119, C120, C121 — 10 nF capacitor  
 C114 — 150 pF capacitor  
 C116, C117, C118 — 1 μF capacitor  
 C122 — C125 — 10 μF capacitor  
 C128 — 1000 μF capacitor  
 C129 — 56 μF capacitor  
 D101 — diode, 1N4148  
 D102 — Zener diode, 6.8 V  
 J101 — microphone jack

J102 — auxiliary jack  
 J103 — RCA jack  
 L101 — 1 mH RF choke  
 Q101 — 2N4416 transistor  
 Q102, Q103 — 2N2222A transistor  
 Q104 — 2N2219A transistor  
 Q105, Q106 — 2N3904 transistor  
 R101, R118 — 180 Ω resistor  
 R102, R130 — 820 Ω resistor  
 R103, R121 — 2.7 kΩ resistor  
 R104 — 1.3 kΩ resistor  
 R105 — 470 kΩ resistor  
 R106 — 51 Ω resistor  
 R107, R115, R122, R123, R134 — 47 kΩ resistor  
 R108, R131 — 100 kΩ resistor  
 R109 — 12 kΩ resistor

R110 — 240 Ω resistor  
 R111, R112, R117, R120, R126, R127, R132, R135 — R137 — 10 kΩ resistor  
 R113, R139 — 5.1 kΩ resistor  
 R114 — 100 kΩ potentiometer  
 R116 — 1.5 MΩ resistor  
 R119, R138, R140 — 1 kΩ resistor  
 R124 — 200 kΩ resistor  
 R125, R129 — 100 Ω resistor  
 R128, R133 — 50 kΩ potentiometer  
 S101 — SPST switch  
 U101 — regulator, 12 V, 7812  
 U102 — balanced modulator, MC1496P  
 U103 — op amp, 741  
 Y101 — 455 kHz resonator  
 Y102 — SSB filter, ceramic 455 kHz, Murata CFWLA455KJFA-B0 ([www.murata.com/products/comm\\_filter/pickup/index.html#if](http://www.murata.com/products/comm_filter/pickup/index.html#if))

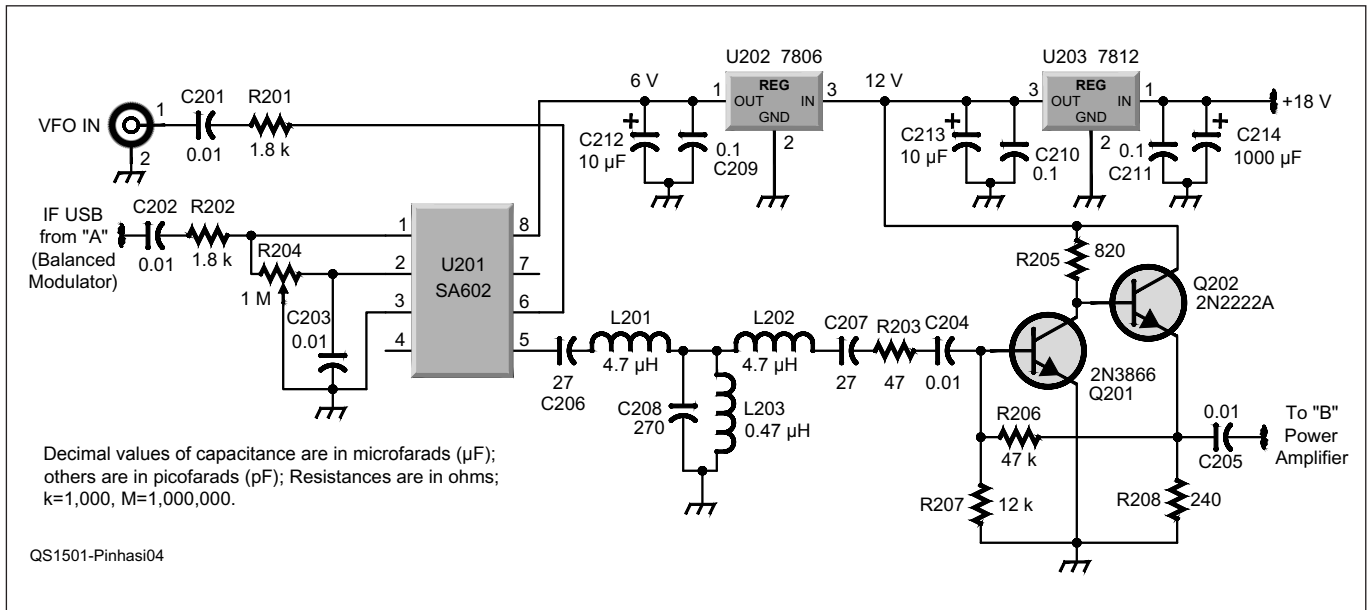

**Figure 4** — Upconversion balanced mixer, RF filter, and driver amplifier.

C201 – C205 — 10 nF capacitor  
 C206, C207 — 27 pF capacitor  
 C208 — 270 pF capacitor  
 C209 – C211 — 0.1 μF capacitor  
 C212, C213 — 10 μF capacitor  
 C214 — 1000 μF capacitor  
 L201, L202 — 4.7 μH inductor

L203 — 0.47 μH inductor  
 Q201 — 2N3866 transistor  
 Q202 — 2N2222A transistor  
 R201, R202 — 1.8 kΩ resistor  
 R203 — 47 Ω resistor  
 R204 — 1 MΩ potentiometer  
 R205 — 820 Ω resistor

R206 — 47 kΩ resistor  
 R207 — 12 kΩ  
 R208 — 240 Ω resistor  
 U201 — balanced mixer, SA602  
 U202 — voltage regulator, 6 V, 7806  
 U203 — voltage regulator, 12 V, 7812

## Power Supply

Figure 7 shows a schematic of my power supply, which is based on a 220 V ac power source. The 250 V and 500 V dc are supplied by a 360 V ac center-tapped 400 mA transformer (on the lower left in Figure 6) via a full wave rectifier D401A-D and filter. Bleeder resistors R401 and R402 discharge capacitors C401 – C404 after the power supply is turned off. It takes approximately one minute until the capacitor voltages decrease to safe values. *Be very careful not to touch hazardous high-voltage terminals during operation.*

A voltage multiplier connected to the 6.3 V ac generates an unregulated 18 V dc for the solid state circuitry. Regulator U401 supplies 5 V to the transmitter cooling fan (visible in Figure 1). The fixed negative bias voltage for V302 tube is obtained by using a small reverse-connected low current 220 V to 12 V transformer. Its 12 V secondary is connected to the 6.3 V ac, attaining above 100 V at the primary. Half-wave rectifier D404 and 47 V Zener diode D406 in series with LED D405 produce –48 V dc. Initially, set the slider of trimmer R403 to ground potential.

## Operation

Turn all the switches OFF. Connect the DDS-VFO and attach a power meter and a dummy load rated for at least 50 W to antenna connector J303 of the transmitter. Turn ON the power mains switches of the transmitter. Allow at least a minute for the tube filaments to warm up. Carefully change the position of bias trimmer R403, raising the voltage until LED D405 lights up. Do not increase the voltage any further. D405 and Zener diode D406 ensure that the voltage is fixed to –48 V and the LED light indicates that the tube is biased properly. Using a voltmeter, verify that the bias of the final power tube grid is stable at the required –48 V.

Supply 250 V (S403) to the driver and 12 V (S404) to the mixer. Tune the VFO to the middle of the 20 meter phone portion of the band (14.230 MHz) and switch ON (S101) the tone oscillator. Rotate the PLATE capacitor to the middle and the LOAD capacitor to the maximum capacitance. Switch ON the transmission (S301) and trim GRID capacitor C310 to obtain the maximum reading on the power meter. Tune the PLATE capacitor to obtain a dip in



the cathode current. Then change the LOAD capacitor to bring the cathode current to a maximum. Readjust C310 to maximum power. In this setting, the output power will be approximately 5 W.

Now turn on the 500 V switch (S402). Slightly readjust the GRID, PLATE and LOAD capacitors to obtain maximum output power. The expected RF output power will be 25 – 30 W PEP, resulting in a 100 – 120 mA cathode current in V302. You do not need to trim C310 anymore, just the PLATE and LOAD. Turn OFF the tone and connect a microphone. During transmission, adjust the modulation level for a maximum PEP at the output without signal clipping.

## Notes

- <sup>1</sup>R. Motorola Semiconductors, Hejhall: "MC1496 Balanced Modulator," Application Note AN531/D, Jan 2002.
- <sup>2</sup>[www.arri.org/qst-in-depth](http://www.arri.org/qst-in-depth)
- <sup>3</sup>Philips Semiconductors, "High sensitivity applications of low-power RF/IF integrated circuits," Application Note AN1993, Aug 2007.
- <sup>4</sup>Philips Semiconductors, "Reviewing key areas when designing with the SA605," Application Note AN1994, Nov 2007.
- <sup>5</sup>D. C. Pongrance: "N3ZI DDS 2," [www.pongrance.com/super-dds.html](http://www.pongrance.com/super-dds.html).

Decimal values of capacitance are in microfarads ( $\mu\text{F}$ ); others are in picofarads (pF); Resistances are in ohms; k=1,000, M=1,000,000.

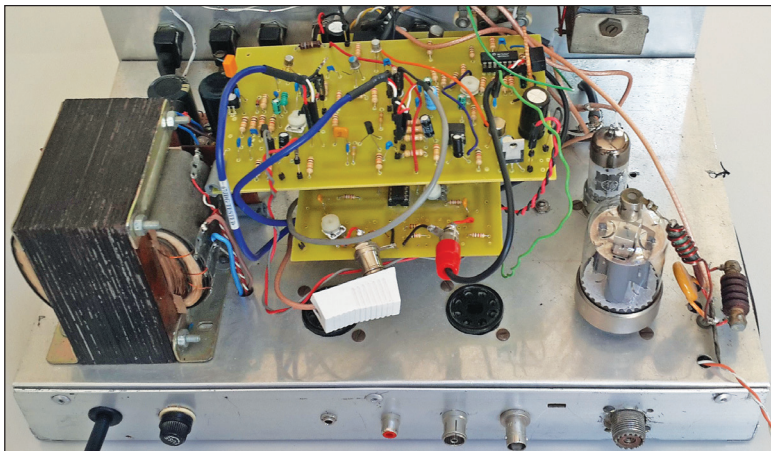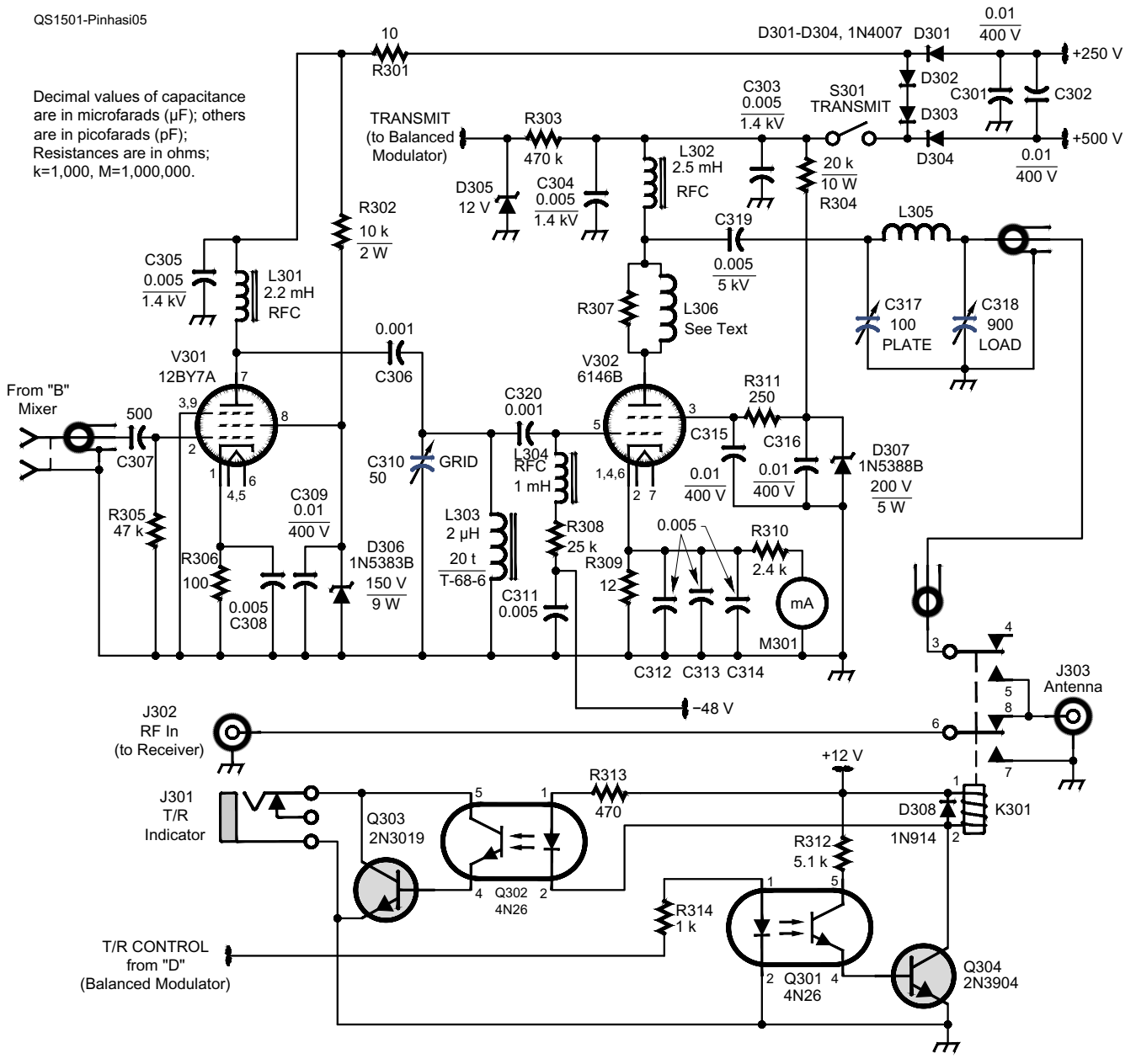

**Figure 6** — Transmitter interior and rear view. The rear connections are (right to left): SO239/ antenna, BNC to receiver, VFO input, IF upper SSB, TR to receiver.


**Figure 5** — The transmitter power amplifier and TR switch schematic.

- C301, C302, C309, C315,
- C316 — 10 nF 400 V capacitor
- C303 – C305, C308, C311 – C314 — 5 nF
- 1.4 kV capacitor
- C306, C320 — 1 nF 1.4 kV capacitor
- C307 — 500 pF 500 V capacitor
- C310 — 50 pF variable capacitor
- C317 — 100 pF variable capacitor
- C318 — 900 pF variable capacitor
- C319 — 5 nF 5 kV capacitor
- D301 – D304 — 1N4007 diode
- D305 — 12 V Zener diode
- D306 — 150 V 5 W Zener diode, 1N5383B
- D307 — 200 V 5 W Zener diode, 1N5388B
- D308 — diode, 1N914
- J301 — phone jack
- J302 — BNC female connector
- J303 — SO239 female connector
- K301 — DPDT relay
- L301 — 2.2 mH RF choke
- L302 — 2.5 mH RF choke
- L303 — 2 μH coil, 20 turns #24 AWG
- on T-68-6 core
- L304 — 1 mH RF choke
- L305 — 7 turns of #16 AWG enameled wire on
- a 3.6 cm diameter plastic cylinder
- L306 — 5 turns of #18 AWG enameled wire
- wound on R307
- M301 — meter, dc 1 mA full scale
- Q301, Q302 — opto-isolator, 4N26
- Q303, Q304 — transistor, 2N3019
- R301 — 10 Ω resistor
- R302 — 10 kΩ 2 W resistor
- R303 — 470 kΩ resistor
- R304 — 20 kΩ 10 W resistor
- R305 — 47 kΩ resistor
- R306 — 100 Ω resistor
- R307 — 47 Ω 1 W resistor, use as coil form for
- L306
- R308 — 25 kΩ resistor
- R309 — 12 Ω resistor
- R310 — 2.4 kΩ resistor
- R311 — 250 Ω resistor
- R312 — 5.1 kΩ resistor
- R313 — 470 Ω resistor
- R314 — 1 kΩ resistor
- S301 — SPST switch
- V301 — miniature pentode vacuum tube
- 12BY7A
- V302 — power tetrode vacuum tube 6146B

Photos by the author.

ARRL member Prof Yosef Pinhasi, 4Z1VC, is the Dean of the Faculty of Engineering at the Ariel University of Samaria. He investigates utilization of electromagnetic waves in a wide range of frequencies for various applications such as communications, remote sensing, and imaging. The space-frequency approach, which he developed, is employed to study propagation of wide-band signals in absorptive and dispersive media in broadband communication links, and wireless indoor and outdoor networks as well as in remote sensing radars operating in the millimeter and Tera-Hertz regimes. He is a member of the Israel Amateur Radio Club (IARC) and can be reached at the Faculty of Engineering, Ariel University, P.O. Box 3, Ariel 40700, Israel, or [yosip@ariel.ac.il](mailto:yosip@ariel.ac.il).

For updates to this article, see the QST Feedback page at [www.arrrl.org/feedback](http://www.arrrl.org/feedback).

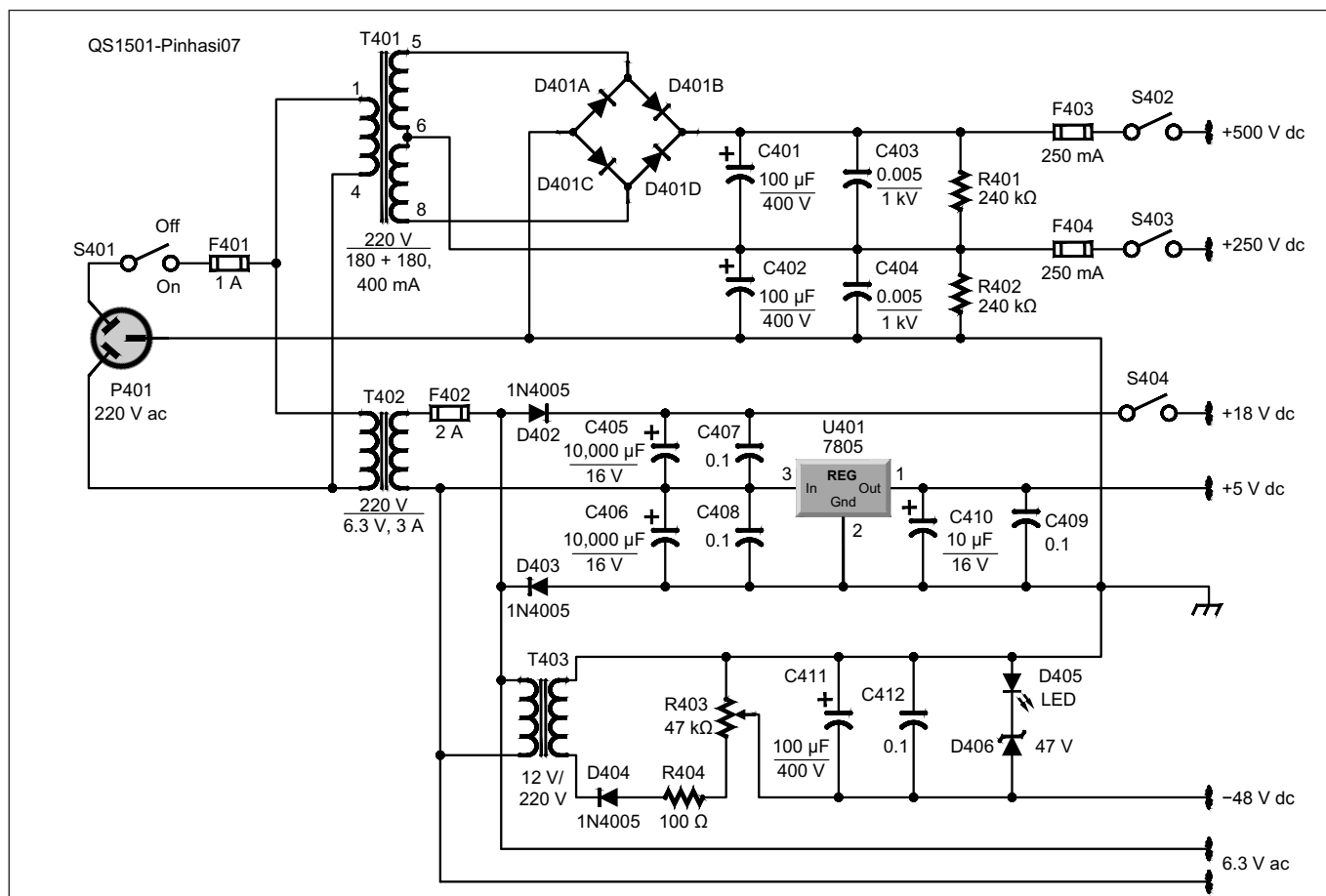

**Figure 7** — The power supply.

- C401, C402, C411 — 100 μF, 400 V capacitor
- C403, C404 — 5 nF, 1 kV capacitor
- C405, C406 — 10,000 μF, 16 V capacitor
- C407 – C409, C412 — 0.1 μF 100 V capacitor
- C410 — 10 μF, 16 V capacitor
- D401A-D401D — full wave diode bridge, or four
- 1N4007 diodes
- D402-D404 — diode, 1N4005
- D405 — LED
- D406 — Zener diode, 47 V
- F401 — fuse, 1 A
- F402 — fuse, 2 A
- F403, F404 — fuse, 250 mA
- P401 — male plug, 220 V ac
- R401, R402 — 240 kΩ resistor
- R403 — 47 kΩ potentiometer
- R404 — 100 Ω resistor
- S401 – S404 — switch, SPST
- T401 — transformer, pri. 220 V ac, sec. 360 V
- ac center tapped
- T402 — filament transformer, pri. 220 V ac, sec.
- 6.3 V ac, 3 A
- T403 — transformer, pri. 12 V ac, sec. 220 V ac
- U401 — voltage regulator, 5 V, 7805.