



Care and
Feeding of
Power Grid
Tubes



CARE AND FEEDING OF POWER GRID TUBES

PREPARED BY THE STAFF OF
CPI, EIMAC DIVISION



Communications & Power Industries

CPI, EIMAC DIVISION
301 INDUSTRIAL ROAD
SAN CARLOS, CA 94070
USA

CARE AND FEEDING OF POWER GRID TUBES

5th Edition

Copyright© 2003 by Eimac Division of CPI, Inc. All rights reserved. Printed in the United States of America. This book, or parts thereof may not be reproduced in any form without permission of the publisher.

Table of Contents

SECTION 1 **1**

INTRODUCTION **1**

SECTION 2 **3**

WHAT IS A POWER GRID TUBE? **3**

2.1 TRIODES 3

2.2 TETRODE 8

2.3 PENTODES 13

2.4 Current Division 14

2.5 INDUCTIVE OUTPUT TUBE (IOT) 16

**2.6 MULTISTAGE DEPRESSED COLLECTOR IOT
(MSDC IOT)** 21

2.7 CATHODE EMITTERS 24

2.8 GRIDS 29

2.9 ANODES 31

2.10 VACUUM PUMPS 32

SECTION 3 **35**

ELECTRICAL DESIGN CONSIDERATIONS **35**

3.1	CLASS OF OPERATION	35
3.2	TUBE PERFORMANCE COMPUTER FOR R-F AMPLIFIERS	37
3.3	TYPICAL RF AMPLIFIER CIRCUIT DESIGNS	52
3.4	COMPONENT PARTS	57
3.5	LEAD LENGTHS	58
3.6	FILAMENT BY-PASSING	60
3.7	SCREEN AND SUPPRESSOR GRID BY-PASSING AND SCREEN TUNING	62
3.8	GROUNDING-GRID CIRCUITS	63
3.9	PROTECTION	65
3.10	KEYING	70
3.11	AMPLITUDE MODULATION	73
3.12	POWER SUPPLY CONSIDERATION	75
3.13	STABILIZING THE AMPLIFIER	76
3.14	NOISE IN TUBE AMPLIFIERS	81

SECTION 4 83

<u>LINEAR AND SINGLE SIDEBAND SERVICE</u>		83
4.1	WHY SINGLE SIDEBAND	83
4.2	RATING TUBES FOR LINEAR AMPLIFIER SERVICE	84

- 4.3 **SELECTION OF TUBES FOR SINGLE SIDEBAND SERVICE 92**
- 4.4 **LINEAR AMPLIFIER DESIGN 100**
- 4.5 **ADJUSTING AND MONITORING THE LINEAR AMPLIFIER 105**

SECTION 5 109

NEUTRALIZATION		109
5.1	NEUTRALIZATION BELOW VHF	109
5.2	PUSH-PULL NEUTRALIZATION	111
5.3	SINGLE-ENDED NEUTRALIZATION	111
5.4	NEUTRALIZING GROUNDED-GRID AMPLIFIERS	113
5.5	NEUTRALIZATION PROCEDURE	117
5.6	SELF-NEUTRALIZING FREQUENCIES OF TETRODES AND PENTODES	120

SECTION 6 125

OPERATING CONDITIONS		125
6.1	ADJUSTMENT OF LOADING AND EXCITATION	125
6.2	OPERATING VOLTAGES AND CURRENTS	126
6.3	EFFECT OF DIFFERENT SCREEN VOLTAGES	127

6.4	THE THREE HALVES POWER LAW	127
6.5	BALANCE OF AMPLIFIERS	128
6.6	HARMONIC AMPLIFIER AND CONTROL OF HARMONICS	130
6.7	SHIELDING	133
6.8	DRIVE POWER REQUIREMENTS	135
6.9	VHF AND UHF OPERATING CONDITIONS FOR SATISFACTORY ANODE EFFICIENCY AND MINIMUM DRIVE	137
6.10	COOLING TECHNIQUES	137
6.11	TUBE LIFE	162

BIBLIOGRAPHY	168
---------------------	------------

Index	169
--------------	------------

Illustrations

Figure 1:	Constant current curves for 3CX3000A1 ($\mu = 5$).	5
Figure 2:	Constant current curves for 3CX3000A7 ($\mu = 160$).	5
Figure 3:	Constant current curves for a zero-bias triode with a μ of 200.	6
Figure 4:	Internal configuration of a planar triode.	7
Figure 5:	Incorrect screen circuit for tube.	10
Figure 6:	A correct screen circuit for tube.	11
Figure 7:	Another approach to swamping the screen circuit.	11
Figure 8:	Typical curve of grid current.	12
Figure 9:	Secondary-emission characteristics of the metals.	13
Figure 10:	Eimac K2 IOT Amplifier	17
Figure 11:	Eimac K2 Inductive Output Tube	19
Figure 12:	Typical tuning curves for UHF TV IOT.	21
Figure 13:	Equipotential lines in a three stage collector.	22
Figure 14:	Electron trajectories at near to ideal power.	23
Figure 15:	Electron trajectories at higher than ideal power.	23
Figure 16:	Typical MSDC IOT power supply schematic	24
Figure 17:	Pulse derating curve.	25
Figure 18:	Typical oxide cathode.	26
Figure 19:	Typical bar tungsten filament.	27
Figure 20:	Typical mesh tungsten filament.	27
Figure 21:	Typical Focus Cathode (LPT-62)	28
Figure 22:	Tungsten Matrix (Dispenser) Cathode.	29
Figure 23:	Anode efficiency vs. Conduction angle.	36
Figure 24:	Variation of anode and grid voltage	38
Figure 25:	Anode voltage and grid voltage scales.	39
Figure 26:	Instantaneous values of anode and grid current.	40
Figure 27:	Constant current characteristics for 4CX20,000A/8990 tetrode.	40
Figure 28:	Constant current characteristics for 4CW100,000D tetrode.	50
Figure 29:	A typical circuit for an RF amplifier.	52
Figure 30:	Relative harmonic vs. Resonant circuit Q.	53
Figure 31:	Determination of input capacitor C1.	53
Figure 32:	Determination of loading Capacitor C2.	54
Figure 33A:	Determination of Inductor L	55
Figure 33B:	Reactance of an RF choke vs. Frequency.	56
Figure 34:	A typical circuit using "zero-bias" triodes.	63
Figure 35:	A typical circuit using "Zero-bias" triodes.	64
Figure 36:	3CX5000A7 with integral grid flange	64
Figure 37:	Tetrode and pentode protection chart.	66
Figure 38:	Triode protection chart.	67
Figure 39A:	Screen voltage control circuit for exciter keying.	71
Figure 39B:	A typical method of keying a tetrode or pentode amplifier.	72
Figure 40:	Basic screen and anode modulation circuits.	73
Figure 41:	Usual circuit supporting VHF parasitic oscillation.	78
Figure 42:	Placement of parasitic suppressors.	79
Figure 43:	Relative spectrum space occupied by AM and SSB signals.	84

Figure 44.	R-F output of SSB transmitter with single-tone modulation.....	85
Figure 45.	Spectrum of SSB transmitter modulated by two-tone signal.....	86
Figure 46.	Spectrum of SSB transmitter modulated by 1500-Hz tone.....	86
Figure 47.	R-f output of SSB transmitter modulated by two-tone signal.....	87
Figure 48.	Single-tone condition.....	89
Figure 49.	Two-tone condition.....	91
Figure 50.	Three-tone condition.....	91
Figure 51.	Spectrum at the output of a non-linear device.....	95
Figure 52.	Ideal grid-anode transfer curve for Class AB operation.....	97
Figure 53.	Block diagram of Intermodulation Distortion Analyzer.....	98
Figure 54.	Intermodulation distortion products may be predicted.....	100
Figure 55.	IM Distortion Test Data for EIMAC 4CX1500B (EC2 = 225V) ...	102
Figure 56.	IM Distortion Test Data for EIMAC 4CX1500B (EC2 = 250V) ..	103
Figure 57.	Wire neutralizing system.....	110
Figure 58.	Push-pull grid neutralization, basic circuit.....	111
Figure 59.	Single-ended grid neutralization.....	111
Figure 60.	Single-ended anode neutralization, basic circuit.....	112
Figure 61.	Single-ended anode neutralization.....	113
Figure 62.	Neutralization of a symmetrical grid-excited amplifier.....	115
Figure 63.	Neutralization by cross-connected capacitors.....	115
Figure 64.	Neutralization by cross-connected capacitors.....	116
Figure 65.	Circuit of grounded-grid amplifier.....	117
Figure 66.	Tetrode characteristics involved in feedback circuit.....	119
Figure 67.	Graphical presentation of components of output circuit.....	119
Figure 68.	Components of output voltage of a tetrode.....	122
Figure 68A.	Components of output voltage of a tetrode.....	123
Figure 69.	Components of output voltage of a tetrode.....	123
Figure 70.	Three-halves power of commonly-used factors.....	128
Figure 71.	Anode-Current Pulse Length and Power Output.....	131
Figure 72.	Typical air cooling system.....	139
Figure 73.	Tube mounting providing cooling, shielding and isolation.....	140
Figure 74.	Chassis mounting providing cooling, shielding and isolation....	140
Figure 75.	Example of a badly overheated tetrode.....	141
Figure 76.	Measuring back-pressure ²⁴	141
Figure 77.	Cooling Airflow Requirements.....	143
Figure 78.	Combined correction factors for land-based installations.....	146
Figure 79.	Conversion of mass airflow rate to volumetric airflow rate.....	147
Figure 80.	Typical vapor-phase cooling system.....	152
Figure 81.	EIMAC vapor-cooled tubes for mounting in boilers.....	152
Figure 82.	Cutaway of "classic" boiler and tube combination.....	153
Figure 83.	Cutaway view of typical Control Box.....	154
Figure 84.	Typical 4-tube vapor cooling system.....	155
Figure 85.	Cutaway of pressure equalizer fitting.....	156
Figure 86.	Typical 4-tube system using "steam-out-the-bottom" boilers....	156
Figure 87.	Cutaway view of "steam-out-the-bottom" boilers.....	159
Figure 88.	Useful conversion factors.....	161